

Ques 1: A) Fill in the blanks by choosing the correct alternative –

(4)

- a) The diode is a _____ current device.
(a) polydirectional (b) unidirectional (c) bidirectional (d) multidirectional
- b) When pentavalent element is mixed with silicon, we get _____ semiconductor.
(a) n-type (b) p-type (c) h-type (d) z-type
- c) The minority charge carriers in N-type semiconductor are _____.
(a) electrons (b) holes (c) +ve ions (d) -ve ions
- d) The energy required to break the covalent bonds in Germanium is _____.
(a) 1.12eV (b) 0.75eV (c) 5.25eV (d) 3.1eV



B) Attempt any TWO of the following –

(6)

- a) In a bridge rectifier circuit, if the turns ratio of transformer is 10:1, with mains voltage of 100V, 50Hz supply, then calculate the output DC voltage of the circuit and its ripple frequency.
- b) Calculate output DC voltage of HWR if the turns ratio of transformer is 100:5, with mains voltage of 200V.
- c) Calculate DC voltage and ripple frequency of FWR if its input AC voltage is 10Vrms at 50Hz.

Ques 2: A) Attempt any TWO of the following –

(6)

- a) Draw circuit diagram of full wave rectifier and explain its working in brief.
- b) Draw circuit diagram of HWR and explain its working.
- c) Calculate the ripple frequency of FWR and HWR, if mains frequency of AC voltage is 55Hz.

B) Attempt any ONE of the following –

(4)

- a) How PN junction diode is forward biased? Explain its working in brief. Also draw the characteristics graph of diode in forward biasing.
- b) Draw circuit diagrams of CC, CB and CE configurations of a transistor.

Ques 3: A) Attempt any TWO of the following –

(6)

- a) What is transistor? Why it is named as transistor?
- b) What is bipolar transistor? Explain the construction of NPN transistor with diagram.
- c) What is hole-electron pair? Explain in brief.

B) Attempt any ONE of the following –

(4)

- a) What is extrinsic semiconductor? Explain in brief.
- b) Write down the electronic configuration of Boron (5), Arsenic (33).

Ques 4: A) Attempt any TWO of the following –

(6)

- a) Derive the mathematical expression between α & β .
- b) Compare p-type and n-type semiconductors.
- c) How p-type semiconductor is formed? Explain in brief with diagram.

B) Attempt any ONE of the following –

(4)

- a) Explain the working reverse biasing of a diode with necessary diagram.
- b) What are the applications of PN junction diode? Give any 2 applications.

Ques 5: A) Attempt any TWO of the following –

(6)

- a) Write down the working of BR with necessary diagram.
- b) Define alpha (α) and (β) of a transistor.
- c) What will happen if any one diode in bridge rectifier is faulty? Explain in brief.

B) Attempt any ONE of the following –

(4)

- a) Write any two advantages of Full wave rectifier.
- b) Write any two advantages of Bridge rectifier.

OR

Ques 5: A) Attempt any TWO of the following –

(6)

- a) Compare HWR, FWR and BR with any three points.
- b) Draw the characteristics graph of PN junction diode and show all the four regions i.e. cut-off region, active region, saturation region and breakdown region in forward biasing condition only.
- c) Write electronic configuration of silicon and germanium.

B) Attempt any ONE of the following –

(4)

- a) What is doping? Explain in brief.
 - b) How PNP transistor is formed? Explain in brief with suitable diagram.
-